

Marks Scored :

KATHMANDU UNIVERSITY  
End Semester Examination  
March/April, 2017

APR 10 2017

Level : B. E.

Course : ETEG 431

Year : IV

Semester : I

Exam Roll No. :

Time: 30 mins.

F. M. : 10

Registration No.:

Date :

SECTION "A"

[20 Q. × 0.5 = 10 marks]

Tick the most appropriate answer for each of the questions below.

- \_\_\_\_\_ transistors in the pull-up network of a NOR gate are connected in \_\_\_\_\_.  
[a] NMOS; parallel [b] NMOS; series [c] PMOS; parallel [d] PMOS; series
- If MOS transistors of same size are used, speed of a 3-input CMOS gate would be \_\_\_\_\_ of that of an inverter.  
[a] half [b] one-third [c] one-sixth [d] one-ninth
- A 1-T DRAM cell stores its data in a \_\_\_\_\_.  
[a] cross-coupled inverter [b] bit line  
[c] capacitor [d] flip-flop
- The threshold voltage of an EPROM transistor increases when the electrons are trapped in:  
[a] drain [b] floating gate [c] channel [d] N-well
- \_\_\_\_\_ memory architecture offers power saving capability.  
[a] Hierarchal [b] Decoder-based [c] Array [d] Linear
- FLASH memory can be regarded as a type of \_\_\_\_\_.  
[a] SRAM [b] Hard-drive [c] EEPROM [d] CPLD
- A PAL with M sum lines and N product lines can have \_\_\_\_\_ unique uncomplemented outputs.  
[a] M [b]  $\log_2(N)$  [c]  $\log_2(M)$  [d] N
- PLA and PROM both have \_\_\_\_\_ arrays.  
[a] programmable OR [b] programmable AND  
[c] fixed OR [d] fixed AND
- Which of the following Verilog procedural block would most likely be inferred as an edge triggered logic with asynchronous reset?  
[a] always @ (posedge clk and negedge rst) [b] always @ (posedge clk or postedge rst)  
[c] always @ (clk\_p or rst\_n) [d] always @ (FDC)

10. If 'B' and 'C' are of 4 bits each, which of the following Verilog statements produces a result that is less than 4 bits in width?  
 [a]  $A = B + C;$  [b]  $A = \{B, C\};$   
 [c]  $A = \{2\{B\}\};$  [d]  $A = \&(B^C);$
11. Which of the following is not a Verilog keyword?  
 [a] forever [b] always [c] repeat [d] again
12. The output of a three-input AND gate can be sensitized to a stuck-at fault at one of the inputs by holding the other two inputs at \_\_\_\_\_.  
 [a] 00 [b] 11 [c] 00 or 11 [d] 01 or 10
13. A fault-free NOR gate presented with a 'zero failing to one' ( $0 \rightarrow 1$ ) at one of its inputs can have either \_\_\_\_\_ or \_\_\_\_\_ at its output.  
 [a]  $0 \rightarrow 1; 1 \rightarrow 0$  [b]  $1 \rightarrow 0; 1 \rightarrow 1$  [c]  $0 \rightarrow 1; 0 \rightarrow 0$  [d]  $1 \rightarrow 0; 0 \rightarrow 0$
14. A static-0 hazard in \_\_\_\_\_ realization can be eliminated by using a redundant \_\_\_\_\_ gate.  
 [a] POS; OR [b] POS; AND [c] SOP; OR [d] SOP; AND
15. Which of the following techniques is used to reduce the area of a digital circuit?  
 [a] Structuring [b] H-tree [c] Parallelism [d] Flattening
16. In fundamental mode circuits, a race condition is non-critical if \_\_\_\_\_.  
 [a] there are two or more stable states in the destination column of the flow table  
 [b] there is only one stable state in the destination column of the flow table  
 [c] there is an unstable state in between the two stable states  
 [d] there is a cycle in between the two stable states
17. Which among the following implementation options has the fastest time-to-market?  
 [a] ASIC [b] FPGA [c] Full Custom [d] Compiled Cell
18. Scan path improves the \_\_\_\_\_ of a sequential circuit.  
 [a] speed and area [b] controllability and observability  
 [c] pipelining stages and parallel blocks [d] fan-in and fan-out
19. Which of the following doesn't contribute to the hold time violations in flipflops?  
 [a] Setup time [b] Logic delay [c] C-to-Q time [d] Clock skew
20. Electromigration \_\_\_\_\_.  
 [a] decreases the reliability of a chip [b] increases the life of a chip  
 [c] increases manufacturing defects in a chip [d] decreases the area of a chip

KATHMANDU UNIVERSITY  
End Semester Examination  
March/April, 2017

APR 10 2017


Level : B.E.  
Year : IV  
Time : 2 hrs. 30 mins.

Course : ETEG 431  
Semester: I  
F. M. : 40

SECTION "B"

Attempt *ANY FIVE* questions. Missing data may be suitably assumed.

 1. a. Construct a complex CMOS gate to realize the Boolean function,  $f = \overline{A + B} \cdot \overline{CD}$ . [3 + 1 + 4=8]
- b. Why are the CMOS gates with large number of inputs not desirable?
- c. Generate a minimal Fault Detection Test Set to cover all stuck-at faults in the circuit given below.



2. a. Distinguish between: [3 + 2 + 3=8]
    - i. ASIC and Full-custom.
    - ii. Gate Array and Standard Cell.
    - iii. Programmable logic array and programmable logic sequencer.
  - b. Implement the logic function,  $f(A,B,C) = AB + C$  in (i) PAL; (ii) PROM.
  - c. What factors contribute towards the power dissipation of a CMOS circuit? What measures can be taken to reduce the power consumption of a CMOS circuit?
3. a. Explain the working of 1-T DRAM with the help of suitable diagram. Compare it with 6-T SRAM. [3 + 3 + 2=8]
  - b. Discuss the use of Floating gate transistors in different types of nonvolatile semiconductor memories.
  - c. Describe Array memory architecture.

4. a. Distinguish between 'reg' and 'wire' Verilog data types.  
 b. Rewrite the following Verilog module to minimize the chip area.

[1 + 2 + 5=8]

```


module eteg ( input [3:0] a,
              input [3:0] b,
              input [3:0] c,
              input sel,
              output wire [7:0] result);
  wire [7:0] res_a;
  wire [7:0] res_b;

  assign result = sel?res_a :res_b;
  assign res_a = a * c;
  assign res_b = b * c;


endmodule

```

 - c. Write a Verilog module to implement the following state diagram. Also, write a Verilog testbench for the module.




 5. a. Distinguish between synchronous and asynchronous sequential circuits. [1 + 2 + 5=8]  
 b. Redesign the circuit,  $f = A\bar{B} + B\bar{C}$  such that the circuit does not produce a static hazard when there is a change in a single input.  
 c. Design a Fundamental mode asynchronous sequential circuit, with one-bit input, that produces the following two-bit output sequence:



where, arrow (→) indicates a change in input. Avoid critical race.

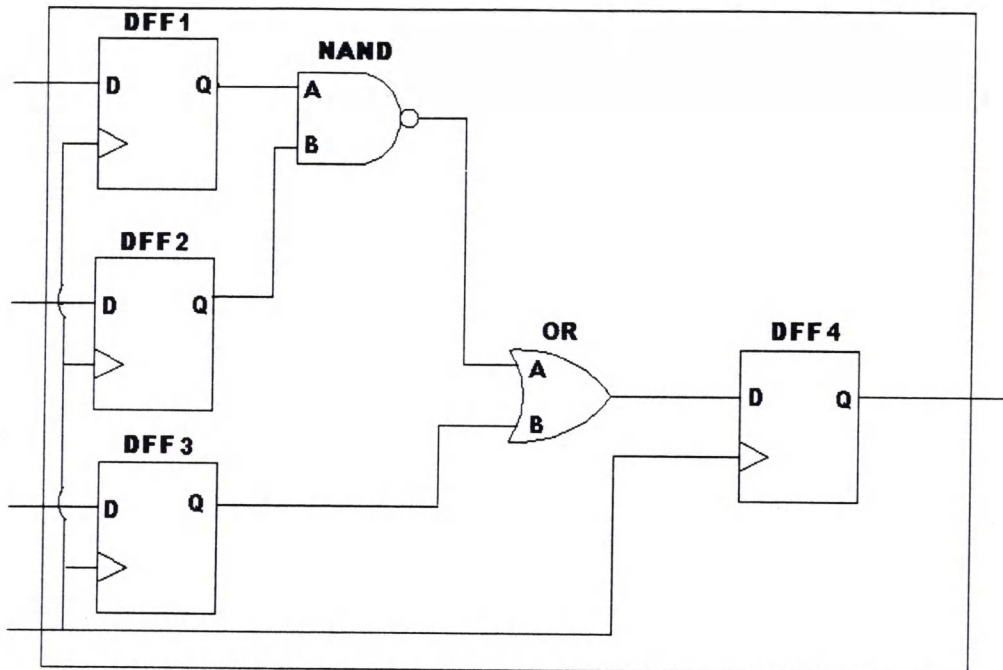6. a. Construct a JK-flipflop with active high asynchronous reset using CMOS pass switches. [3 + 1 + 4=8]  
 b. Why does a CMOS gate have different slew rates?  
 c. Consider the circuit given below. Clock skew is 0.004ns. Setup time and hold time for the flipflops are 0.007ns and 0.008ns respectively. Delay in the wires is negligible. Other parameters are given in the table below. Determine the maximum clock frequency of the circuit. Also, check the circuit for hold time violation.



DATA					
NAND		OR		DFF	
Input Load:		Input Load:		Input Load:	
Pin Name	Load (fF)	Pin Name	Load (fF)	Pin Name	Load (fF)
A	3.2	A	3.5	D	2.9
B	3.4	B	3.8		
Slew Factor:		Slew Factor:		Slew Factor:	
Factor (ns/fF)	0.03	Factor (ns/fF)	0.04	Factor (ns/fF)	0.02
Constant (ns)	0.05	Constant (ns)	0.06	Constant (ns)	0.04

